

EE-474 Distribution Systems Term Project – 3

Aim: Simulate the defined network under the specified conditions in PSS/Sincal environment.

- 34.5 kV infinite bus supplies a load of 30 MW.
- Cable: $240 \times 3 + 25 \text{ mm}^2$ (copper)
- Connectivity:
 - Supply – DT-1: 2 km
 - DT-1 – DT-2: 2 km
 - DT-2 – DT-3: 3 km

Tasks:

- 1) Determine the load voltages and losses for the following cases.
 - a. The load is demanded at DT-3.
 - b. The load is demanded at DT-1
 - c. The load is equally distributed to DT-1, DT-2 and DT-3.
- 2) Assume there exists another DT (DT-4), such that DT-4 is connected to DT-2 via 2-km-long cable (same type). Load is distributed as follows:
 - DT-1: 10 MW
 - DT-2: 10 MW
 - DT-3: 5 MW
 - DT-4: 5 MWDetermine the load voltages and losses.
- 3) Report your findings (Discuss your results, compare found values, etc.).

Results:

- You should submit all reports via ODTUClass in pdf format.
- State all references and sources you used (books, papers, online tools, websites, etc.).
- Format of the reports are also graded. Pay attention to the formal writing rules.
- No late submission is allowed.